



‘समाजो मन्त्रः समितिः समानी’

UNIVERSITY OF NORTH BENGAL

B.Sc. Honours 4th Semester Examination, 2023

CC10-PHYSICS

ANALOG SYSTEMS AND APPLICATIONS

Time Allotted: 2 Hours

Full Marks: 40

The figures in the margin indicate full marks.

GROUP-A

1. Answer any **five** questions from the following: $1 \times 5 = 5$
- (a) “Si is preferred material over Ge in electronic devices” — Justify.
 - (b) Which charge carriers have higher mobility and why?
 - (c) A transistor connected in CE mode has $\alpha = 0.99$. Calculate the β value. The symbols carry their usual meaning.
 - (d) What do you mean by load line of a transistor?
 - (e) The temperature co-efficient of zener breakdown voltage is negative. Explain it.
 - (f) What is Barkhausen criterion for a feedback amplifier to function as an oscillator?
 - (g) Mention few advantages of using negative feedback amplifiers.
 - (h) Draw a neat circuit diagram of a bridge rectifier.

GROUP-B


Answer any three questions from the following

$5 \times 3 = 15$

2. (a) Why determination of Q point is important for a transistor amplifier? 1
- (b) Discuss the input and output characteristics of a CE p-n-p transistor. 2+2
3. (a) Explain the conduction process for extrinsic semi-conductor using band theory of solids. 3
- (b) Determine the conductivity of pure Ge at 300 K. Assume the intrinsic carrier concentration is $2.5 \times 10^{19} \text{ m}^{-3}$, electron's mobility = $0.375 \text{ m}^2/\text{V.s}$ and hole's mobility = $0.175 \text{ m}^2/\text{V.s}$. 2
4. Give a neat circuit diagram of Wien bridge oscillator and explain how it works. Show that the voltage gain of the amplifier used in this oscillator must be greater than 3. 1+2+2

5. (a) With a neat sketch, describe the construction of n-channel JFET. Describe its principle of operation. 2+2
 (b) What are the advantages of using FET over BJT? 1

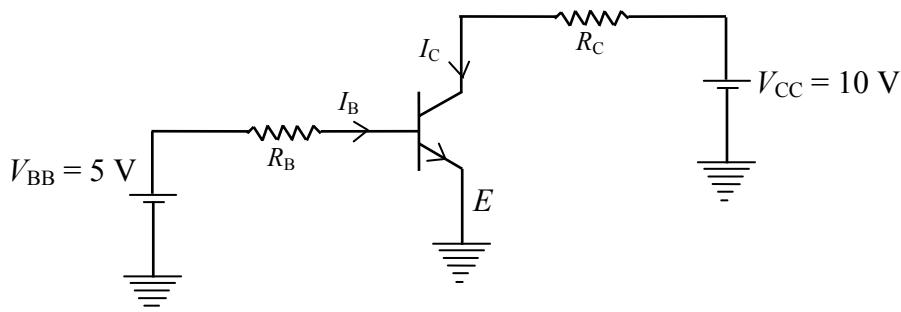6. (a) In a transistor, can the emitter be used as collector and vice-versa? — Explain. 2
 (b) Consider the circuit given below. Find the value of R_B and R_C required to operate the transistor at $I_C = 1 \text{ mA}$ and $V_{CE} = 5 \text{ V}$. Assume $\beta_{d.c} = 100$ and $V_{BE} = 0.7 \text{ V}$. 3



GROUP-C

Answer any two questions from the following

$10 \times 2 = 20$

7. (a) Derive an expression for the width of depletion region across a p-n junction in terms of impurity concentration. 4
 (b) Calculate the ratio of the current for a forward bias of 0.06 V to the current for the same value of reverse bias applied to a Ge p-n diode at 27°C ($\eta = 1$). 3
 (c) What do you mean by static and dynamic resistance of a diode? How does dynamic resistance vary with current and temperature? 1+1+1
8. (a) What are the fundamental differences among the class A, class B and class C amplifiers? 3
 (b) Draw the circuit of RC coupled amplifier. Obtain an expression for the voltage gain in mid-frequency range. 2+5
9. (a) Calculate the closed loop gain of a voltage amplifier using negative feedback. 3
 (b) In a phase shift oscillator $R = R_L = 1 \text{ m}\Omega$ and $C = 75 \text{ pF}$. At what frequency does the circuit oscillate? 3
 (c) Show that the intrinsic carrier concentration is proportional to $T^{3/2} e^{-Eg/2kT}$. 4
- 10.(a) Explain how an OPAMP may be used as, (i) Differentiator, (ii) Integrator. For each case, mention the modifications required to use the devices for practical purpose, with proper circuit diagram. 2+2+
 $1\frac{1}{2} + 1\frac{1}{2}$
 (b) Draw a circuit using one or more OP-AMP whose output v_0 is given as $v_0 = 4v_1 + 6v_2$, where v_1 and v_2 are two input signals. 3

—x—