



'समानो मन्त्रः समितिः समानी'

UNIVERSITY OF NORTH BENGAL
B.Sc. Honours 4th Semester Examination, 2022

CC10-PHYSICS

ANALOG SYSTEMS AND APPLICATIONS

Time Allotted: 2 Hours

Full Marks: 40

*The figures in the margin indicate full marks.
All symbols are of usual significance.*

GROUP-A

1. Answer any **five** questions from the following: 1×5 = 5
- (a) At a high temperature an extrinsic semiconductor behaves like an intrinsic semiconductor. — Explain.
 - (b) For a certain transistor with $\alpha_{dc} = 0.98$ and emitter current $I_E = 2 \text{ mA}$, calculate the base current.
 - (c) What is the virtual ground of an operational amplifier?
 - (d) What is the open loop gain of an operational amplifier?
 - (e) What do you mean by the term 'avalanche breakdown' of a p-n junction diode?
 - (f) What do you mean by the term Q -point of a transistor?
 - (g) In a half wave rectifier, the peak value of the ac voltage across the secondary of the transformer is $20\sqrt{2}$ volt. If, no filter circuit is used, calculate the maximum dc voltage across the load.
 - (h) Draw the voltage transfer characteristics (VTC) of a Schmidt trigger circuit.

GROUP-B

Answer any three questions from the following 5×3 = 15

2. (a) Explain the use of Zener diode as a voltage regulator with suitable circuit diagram. 4
- (b) Write down the voltage-current relation in a p-n junction diode in forward bias condition. 1
3. (a) Draw the energy-band diagram of a p-n junction diode and indicate the locations of donor level, acceptor level and fermi energy level in this diagram. 3

- (b) Calculate the values of dc resistance and ac resistance of a germanium p-n junction diode at temperature 27°C for applied voltage 0.1 volt, reverse saturation current $I_0 = 20 \mu\text{A}$ and ratio of Boltzmann constant to electric charge of an electron $= \frac{k_B}{e} = \frac{1}{11600}$. 2
4. (a) Draw the diagram of the voltage divider biasing circuit in transistor and derive the expression of the base current I_B . 3
- (b) Show that the value of stability factor for the voltage divider biasing method approaches to unity. 2
5. (a) Show that negative feedback in amplifiers can improve the stability of an amplifier. 1 $\frac{1}{2}$
- (b) Show that negative feedback can change the input impedance of an amplifier. 1 $\frac{1}{2}$
- (c) Explain why common emitter configuration is preferred for amplifier design. 2
6. (a) Draw a net diagram of a RC-phase shift oscillator. 2
- (b) Write down the expression for frequency of oscillation in RC-phase shift oscillator. (Derivation is not needed). 1
- (c) Why three identical R-C sections are used in R-C phase shift oscillator? 2

GROUP-C

Answer any *two* questions from the following


10×2 = 20

7. (a) Draw and label the circuit diagram of a small signal single stage low frequency transistor amplifier in the CE mode. 2+1+1+1+2

Using the h parameters, obtain the expressions of current gain, input impedance, voltage gain and output impedance of this transistor amplifier.

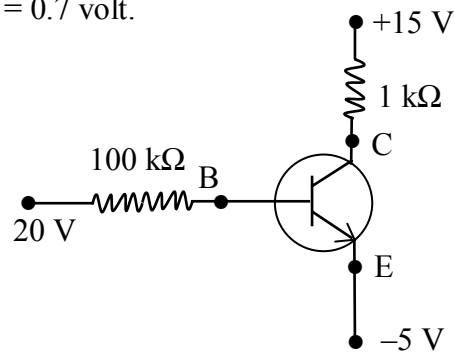- (b) Calculate the values of I_B , I_C , I_E and V_{OE} for the transistor circuit given below. 3

Assume, $\beta = 50$, $V_{BE} = 0.7$ volt.



8. (a) Derive the expression of output voltage for inverting amplifier with proper circuit diagram. 4

- (b) Why inverting amplifier circuit is also known as 180° phase shifter circuit? 1
- (c) Show that the electrical mobility of the electrons in a semiconductor is $\mu = \frac{e\tau}{m^*}$, where the symbols have their usual meanings. 3
- (d) What are the differences between Field Effect Transistor (FET) and Bipolar Junction Transistor (BJT)? 2
9. (a) Draw the circuit diagram of a full wave bridge rectifier using semiconductor diodes. 2+4
 Find out the expressions of Ripple factor and Rectification efficiency of this full wave bridge rectifier.
- (b) The band gap of a specimen of gallium arsenide phosphide is 1.98 eV. 2
 Determine the wavelength of the electromagnetic radiation that is emitted upon direct recombination.
 What is the colour of the emitted radiation?
- (c) State and explain the Barkhausen criterion for an oscillator. 2
- 10.(a) Explain the operation of an OPAMP as a 3+3
 (i) Differentiator
 (ii) Integrator.
- (b) What should be the input resistance, output resistance, voltage gain and band width of an ideal OPAMP? 2
- (c) At the temperature 300 K, the intrinsic carrier concentration of silicon is $1.5 \times 10^{16} \text{ m}^{-3}$. 2
 If the electron and the hole mobilities are $0.13 \text{ m}^2\text{v}^{-1}\text{s}^{-1}$ and $0.05 \text{ m}^2\text{v}^{-1}\text{s}^{-1}$ respectively, determine the value of intrinsic resistivity of the silicon at temperature 300 K.

—x—