



'समानो मन्त्रः समितिः समानी'

**UNIVERSITY OF NORTH BENGAL**

B.Sc. Sec 1st Semester Examination, 2023

**UPHYSEC11001-PHYSICS**

**BASIC ELECTRICAL CIRCUITS AND MEASUREMENTS**

Time Allotted: 2 Hours

Full Marks: 40


*The figures in the margin indicate full marks.*

**GROUP-A**  
**(Compulsory)**

1. Choose the correct alternative: 1×5 = 5

(a) The current  $I$  in the given circuit is

- (A) 2 A
- (B) 3 A
- (C) 4 A
- (D) 5 A

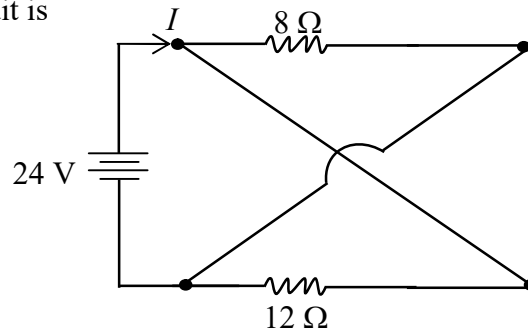

(b) An ammeter with full scale deflection current of  $100 \mu\text{A}$  and internal resistance of  $100 \Omega$  is required to measure a maximum current of  $10 \text{ mA}$ . The shunt resistance needed is

- (A)  $1 \Omega$
- (B)  $1.01 \Omega$
- (C)  $10 \Omega$
- (D)  $10.1 \Omega$

(c) Following figure represent a



- (A) heater
- (B) fuse
- (C) circuit breaker
- (D) switch

(d) Which type of flux does transformer action need?

- (A) Alternating electric flux
- (B) Alternating magnetic flux
- (C) Increasing magnetic flux
- (D) Constant magnetic flux

(e) For a coil with inductance  $L$  and resistance  $R$  in series with a capacitor  $C$  has resonance impedance:

- (A) zero
- (B)  $R$
- (C)  $\frac{L}{CR}$
- (D) infinity


**GROUP-B**

Answer any *three* questions from the following


5×3 = 15

2. In the circuit shown, the voltage source follows the law  $V(t) = V_0 e^{-\alpha t}$ , where  $V_0, \alpha$  are constants. The switch is closed at  $t = 0$ . Solve for the current, when (i)  $\alpha = \frac{R}{L}$  and (ii)  $\alpha \neq \frac{R}{L}$ . 5

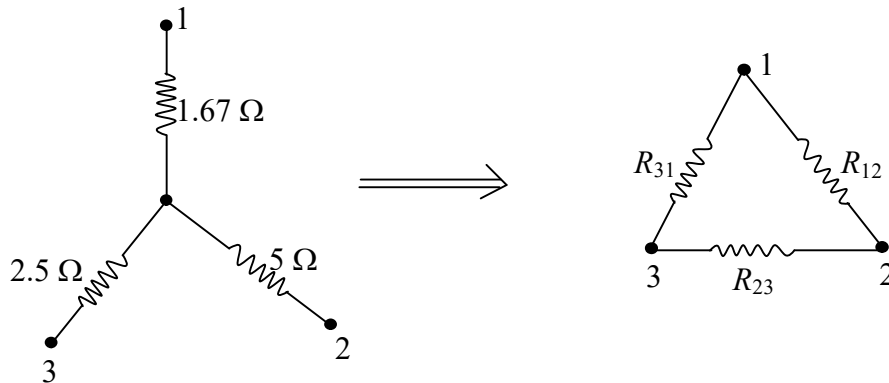3. A star type connection of resistance as shown in figure is converted to an equivalent delta-type configuration. Determine the resistance ( $R_{12}, R_{23}, R_{31}$ ) between the terminal of delta-type system. 5



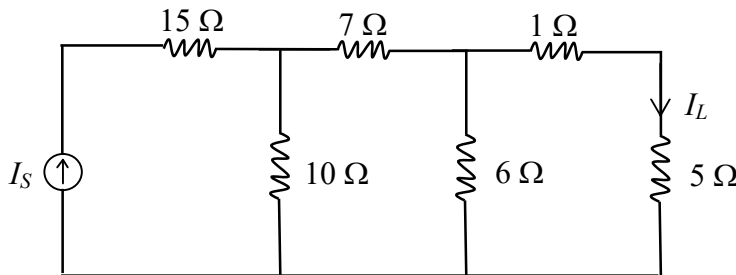4. (a) State Ohm's law. Define resistivity. 2  
 (b) Find the ratio  $\frac{I_L}{I_S}$  in the following circuit. 3




5. (a) Define Complex Power. 1  
 (b) Complex power for a circuit is given by  $S = 100 + j50 \text{ VA}$ . Find the (i) apparent power and (ii) power factor. 2+2
6. (a) What do you mean by impedance of a circuit? 1  
 (b) A voltage  $V = (8 + 6j) \text{ V}$  is applied to a circuit. The resulting current is  $I = (3 - 4j) \text{ A}$ . Find the (i) impedance and (ii) values of circuit element if the circuit is connected across an a.c. source of frequency 50 Hz. 2+2
7. Draw the circuit diagram of a full wave bridge rectifier and explain its operation. 2+3

**GROUP-C**

**Answer any two questions from the following**

10×2 = 20

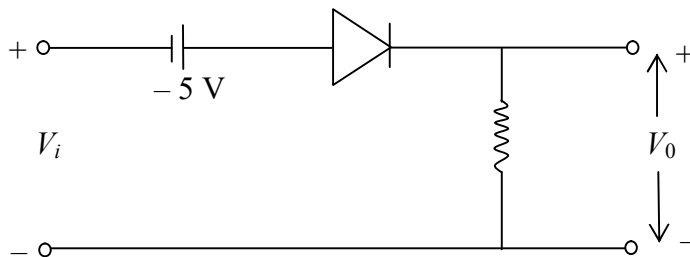8. (a) Describe in brief the construction and explain principle and operation of a permanent magnet moving coil (PMMC) instrument. 5
- (b) How will you use a PMMC instrument which gives full scale deflection at 50 mV P.d and 10 mA current as 2+2
- (i) a Voltmeter of 0-250 V range?
- (ii) an Ammeter of 0-10 A range?
- (c) Can you measure power in an a.c. circuit by using an ammeter and a voltmeter? Justify your answer. 1
9. (a) Why is the three phase voltage system preferred for supplying power? 2
- (b) Derive the relation between phase and line voltage and phase and line current for a balanced three-phase Y connected load (star-connected). 5
- (c) A balanced three phase Y connected load is fed from a 400 V, three phase, 50 Hz supply. The current per phase is 25 A and total active power absorbed by the load is 13.856 kW. Calculate the power factor. 3
- 10.(a) State the condition for maximum efficiency of a D.C. generator. 3
- (b) Derive an expression for the frequency of the generated emf in an AC generator. 4
- (c) What do you mean by synchronous generator? Between DC and AC generator which one falls in this category and why? 1+2
- 11.(a) What is the function of insulator in transmission line? 2
- (b) Give the schematic representation of (i) photodiode and (ii) overload safety switch. 2
- (c) What is ground fault protection? 2
- (d) Determine the output wave form of the given circuit when  $V_i = 20\sin \omega t$  and  $R = 100\Omega$ . 3



- (e) What is the polar representation of the voltage  $(\sqrt{3} + j) V$ ? 1

—x—