



'সমানো মন্ত্র: সমিতি: সমানী'

UNIVERSITY OF NORTH BENGAL

BCA Major 1st Semester Examination, 2023

UBCAMAJ11001-BACHELOR OF COMPUTER APPLICATION

DIGITAL ELECTRONICS

Time Allotted: 2 Hours

Full Marks: 40

The figures in the margin indicate full marks.

GROUP-A

1. Answer any **five** questions from the following: 1×5 = 5
- (a) What are the different logic gates available?
 - (b) Define a flip flop.
 - (c) Convert $(10001101)_2$ into its decimal equivalent.
 - (d) State De Morgan's theorem.
 - (e) Write down two applications of a multiplexer.
 - (f) What is a ripple counter?
 - (g) Write down the characteristic equation of a D flip flop.
 - (h) Expand CMOS.

GROUP-B

2. Answer any **three** questions from the following: 5×3 = 15
- (a) Minimize the given function using K-map
 $f(A,B,C) = \Sigma (1, 2, 3, 5, 7)$
 - (b) (i) Prove that $(A + B)(\overline{A\overline{C}} + C)(\overline{\overline{B} + AC}) = \overline{A}B$.
 (ii) Add $(11110111)_2$ with $(10011111)_2$
 - (c) Implement a half adder using two full adders.
 - (d) What is a decoder? Explain with the help of a truth table and circuit diagram.
 - (e) What is a S-R flip flop? Explain. How can we convert it to a D-flip flop?

GROUP-C

3. Answer any **two** questions from the following: 10×2 = 20
- (a) What are universal gates? Name one and explain why it is called a universal gate.
 - (b) Discuss the working of a J-K flip flop with a proper diagram. What is the problem faced in a J-K flip flop?
 - (c) What are shift registers? What are the different types of shift register? Explain.
 - (d) What is a 16×1 multiplexer? Implement a 16×1 multiplexer using two 8×1 multiplexers.

—×—